

- [Introduction](#)
- [Memory](#)
- [ALU block](#)
- [CPU](#)
 - [ALU command](#)
 - [JUMP command](#)
- [Full program](#)
 - [Multiplication](#)
 - [Multiplication program](#)
 - [Multiplication simulation](#)
 - [Fibonacci sequene](#)

Introduction

In this document, we will go through some simulation to see the functionality of the subblocks for better understanding their functions. Then we will be introduced about 2 full programs to see how the whole system works.

Run simulation with command:

```
run.csh <vector>
```

The output of simulation:

```
compile.log      # The log file for the last compilation
sim_<vector>.log # The simulation log file for the vector
<vector>.fsdb    # The waveform of the simulation
```


When verifying the submodules, the testbench will try to "force" the inputs so that it can monitor the output without the need of activating all other blocks.

Memory

In this test, we try to verify the memory by writing and reading data. Through this test, we can also verify the functionality of the common `register` module.


- Randomize data & address 16 times, then write to the memory
 - In each step, enable address register to capture the address. (We assure that there is no duplicate address in this step)
 - Then enable data to capture the data.

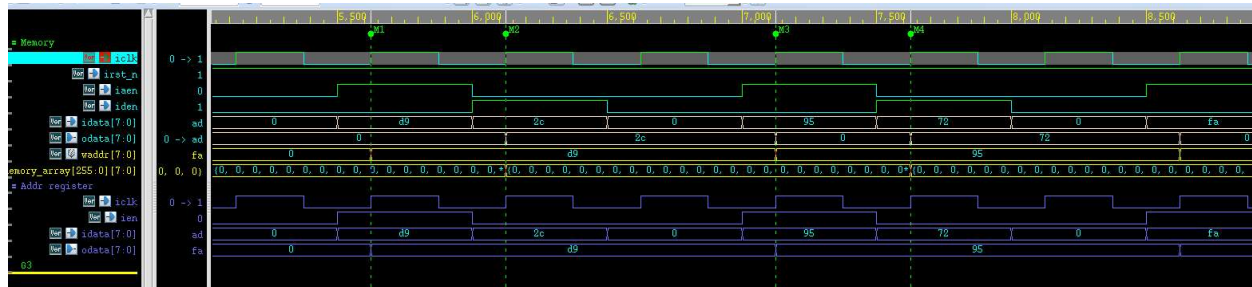- Read all 16 addresses in previous step and compare with the written data to see if it is stored correctly or not.
 - In each step, enable address register to capture the address.
 - Compare the data on the memory's output with the written data.



In the figure above, M1 & M3 are where we store the address. The signal waddr (yellow color) is the output of the address register. Whenever the signal iaen asserts, the signal changes to the value of idata. The blue signals are the ones from Address register (which is common module).

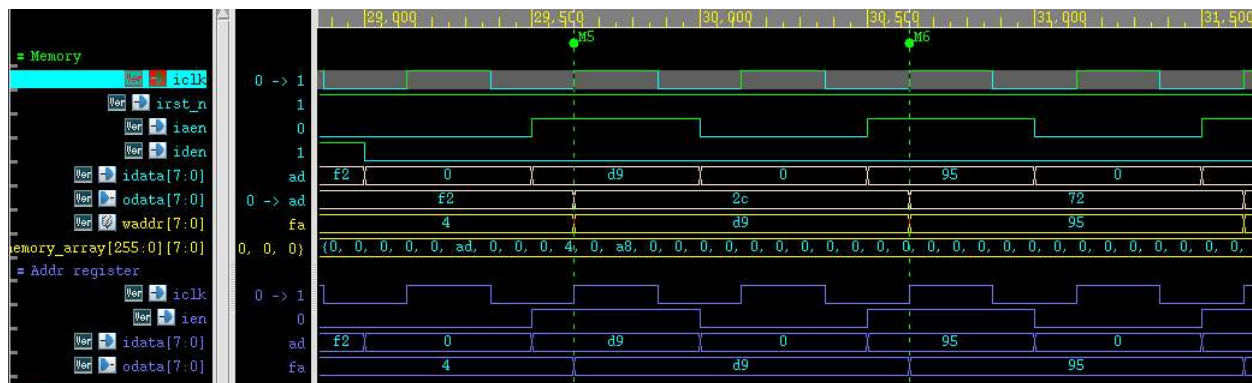The markers M2 & M4 are the time we store data into the memory array (yellow color). The array updates value whenever iden signal asserts.



In above figure, the output of the memory odata updates whenever the address register gets new value in M5 & M6. And the output's value is what we written previously on M2 & M4

ALU block

In this test, randomize will be hard to show the functionality of the block. Thus, the testbench use direct test method:


- ADD 255 & 1. Expect to see result 0 with flags carry 1, zero 1
- Right shift 3. Expect to see result b1000_0001 with flag carry 1. The previous step creates carry flag to be 1, thus it affects the result of this step.
- ADD 5 with force RB to be 1. We expect the carry in previous step doesn't affect this step because it should be AIR calculation; the output increase 1 no matter what value RB is.

The steps to run this testbench follows CPU's order:

- [illegible]


CPU

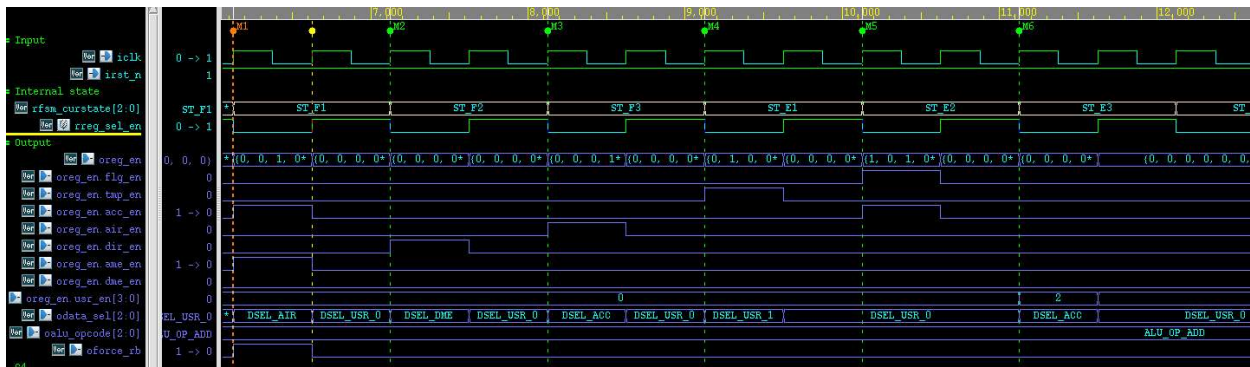In this test, we assign ALU ADD instruction into the CPU and monitor the operation on the outputs.




- ## JUMP command

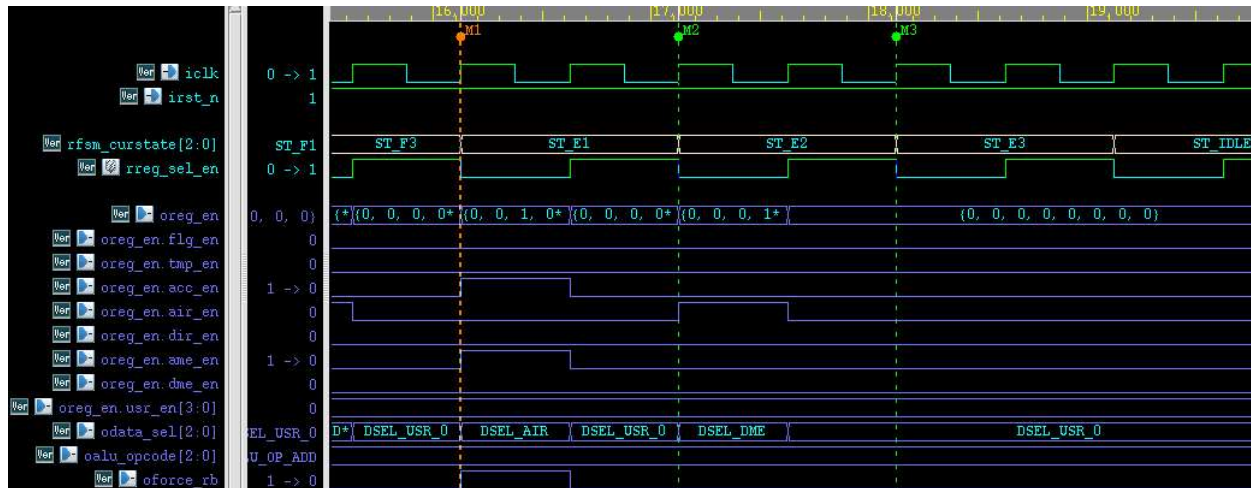The JUMP commands require 2 memory addresses instead of 1, and the final value of AIR depends on the flags' comparison.



The Fetch states stay the same across instruction, below are the Execute states when flag matching is good:

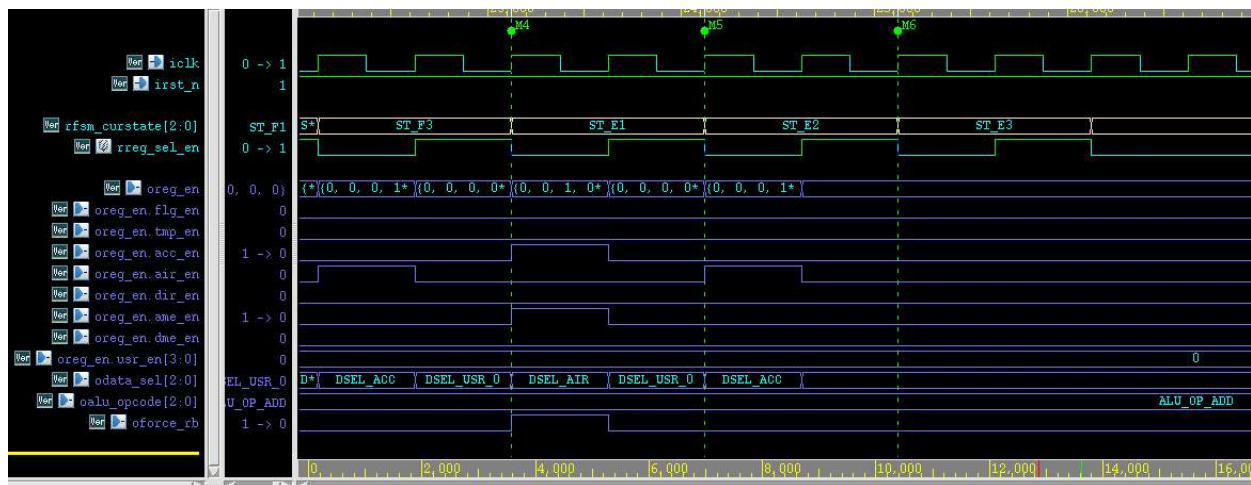- AME is enabled at ST_E1 (see ame_en), the data is from AIR that is calculated in the previous state. In this state, the signal acc_en doesn't affect if the flag is matched.
- AIR captures the data from memory in ST_E2.
- CPU doesn't do anything in ST_E3 for this instruction.



In the case the flags are not matched, CPU change the source of data in ST_E2. The port odata_sel now select accumulator block instead of memory. The accumulator gets the new value in ST_E1, where the ALU is forced ADD 1.

Full program

In this section, we will go through some program to see how the whole system works. Simulation will need to use *force ... release* syntax to write the program into the memory before enabling the CPU.

Multiplication

Multiplication program

Multiplication in binary is just like in decimal, example:

```
  00001011
* 00000101
-----
  00001011
 00001011
-----
 00110111
```

To make it to be a program, first we put the 2 numbers into 2 variable V1, V2, and the result is V3. The step will be:

- Step 1: Check LSB of V2, if it is 1, then $V3 = V1 + V3$
- Step 2: Leftshift V1, Rightshift V2
- Step 3: Repeat from Step 1 until we shift all bits.


From above algorithm, we use R0, R1 and R2 to be the 3 variables. We also need R3 to be the bit counter, that make sure we only shift 8 bits. In this program, we do a little different by doing Rightshift V2 in step 1, so that we can check the value by using carry flag in the ALU.

Program: [Multiply](#)

Multiplication simulation


The first command of the program:

```
DATA R0 11 # First number
```

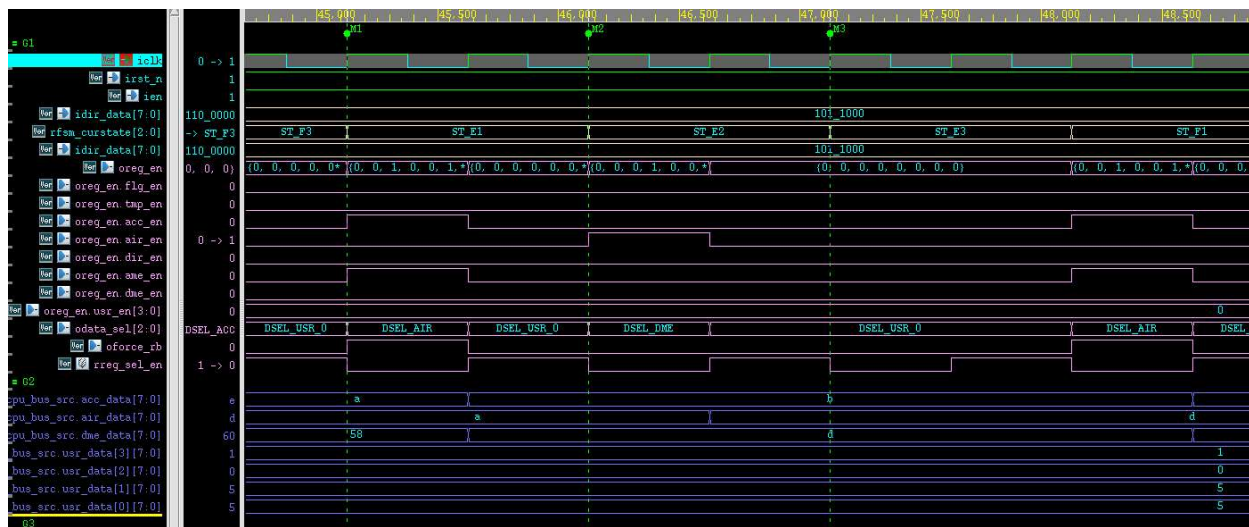- **ST_E1:**
 - AIR is holding value from the state ST_F3, AME is enabled so to get data on that address.
 - ACC is not used in this case.
- **ST_E2:**
 - AIR is enabled to capture data from memory
 - By this time, AIR "jumps" to another address rather than increases 1 step like normal commands.
- **ST_E3:** Idle state

 During the program runs, R2 updates value twice. The first time is b1011, the second time si b110111 (55 in decimal). Which is expected value of the program.



Fibonacci sequence

The Fibonacci sequence is a sequence in which each number is the sum of the two preceding ones.

In our CPU, the ADD command adds RA and RB, then store the data into RB:

- We always need bigger number is in RA, because that information is used for the next ADD command.
- However, the result is stored in RB, which is the bigger value after the command.

Solution:

- RA ADD RB
- Store RA and RB into 2 addresses
- Swap RA and RB by loading the 2 addresses in to RB and RA
- Repeat the ADD command until carry flag asserts

Program: [Fibonacci](#)